
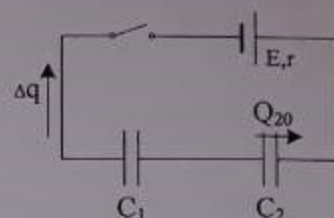


1. U kolu na Slici 1 poznato je $C_1 = C_2 = 40 \text{ mF}$, $E = 16 \text{ V}$, $r = 1 \Omega$. Prekidač je otvoren, a kondenzator C_2 je opterećen početnom količinom naelektrisanja $Q_{20} = 80 \text{ mC}$. Odrediti količinu naelektrisanja Δq koja će proteći kroz kolo, nakon zatvaranja prekidača. Označiti referentne smerove i odrediti napon na kondenzatoru C_1 i količinu naelektrisanja na kondenzatoru C_2 nakon uspostavljanja stacionarnog stanja. (20 poena)

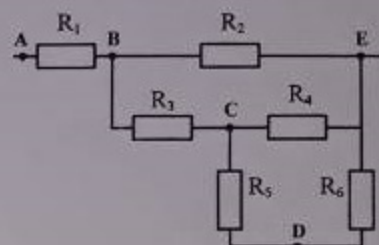


Slika 1

2. Na Slici 2 prikazana je grupa od šest jednakih otpornika, $R_1 = R_2 = R_3 = R_4 = R_5 = R_6 = R = 6 \text{ m}\Omega$. Odrediti ekvivalentnu otpornost između tačaka D i C. (15 poena)



Slika 2


3. Na Slici 3 prikazano je magnetno kolo sa dva namotaja. Namotaj sa N_1 navojaka je otvorenih krajeva, a kroz namotaj sa N_2 navojaka protiče struja intenziteta $i(t) = I_m \cos \omega t$. Jezgro je homogeno i sastoji se iz dva dela površina poprečnog preseka S_1 i S_2 , čije dužine srednjih linija iznose l_1 i l_2 . Magnetna permeabilnost jezgra iznosi μ .

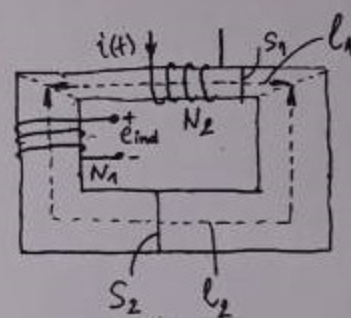

Slika 3


- Odrediti intenzitet vektora jačine magnetnog polja u delu jezgra dužine l_2 . (10 poena)
- Odrediti sopstvenu induktivnost namotaja sa N_2 navojaka. (5 poena)
- Odrediti efektivnu vrednost elektromotorne sile indukovane na krajevima namotaja sa N_1 navojaka. (10 poena)

4. Na Slici 4 prikazan je trofazni sistem generator-potrošač. Efektivna vrednost elektromotornih sila iznosi $E = 300 \text{ V}$, prividna snaga potrošača $S = 4.5 \text{ kVA}$, a reaktivna snaga $Q = -3.6 \text{ kvar}$. Odrediti efektivnu vrednost linijske struje i kompleksnu impedansu potrošača. (20 poena)

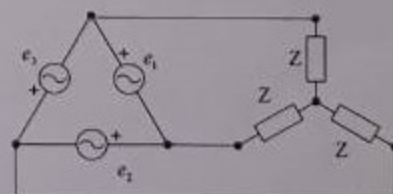

Slika 4

5. U kolu na Slici 5 poznate su vrednosti elemenata: $E = 24 \text{ V}$, $R_1 = R_2 = R_3 = 3 \Omega$ i $L = 6 \mu\text{H}$. Prekidač se nalazi u položaju (2) i u kolu je uspostavljeno stacionarno stanje. U trenutku $t = 0$, prekidač se prebacuje u položaj (1).

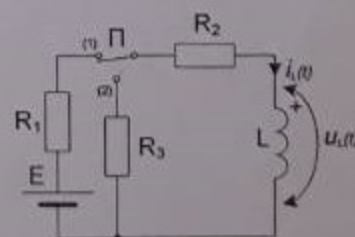

Slika 5

- Odrediti izraze za struju i napon kalema nakon prebacivanja prekidača i nacrtati odgovarajuće vremenske dijagrame. (15 poena)
- Odrediti u kom trenutku će struja kalema imati vrednost $i_L(t_X) = 3 \text{ A}$. (5 poena)

① $C_1 = C_2 = 40 \text{ mF}$, $E = 16 \text{ V}$, $r = 1 \Omega$, $Q_{20} = 80 \text{ mC}$

$\Delta Q = ?$ $C_1 = \frac{Q_1}{U_1} = \frac{\Delta Q}{U_1} \Rightarrow U_1 = \frac{\Delta Q}{C_1}$

$U_1 = ?$

$Q_2 = ?$ $C_2 = \frac{Q_2}{U_2} = \frac{\Delta Q - Q_{20}}{U_2} \Rightarrow U_2 = \frac{\Delta Q - Q_{20}}{C_2}$

$U_1 + U_2 = E$

$\frac{\Delta Q}{C_1} + \frac{\Delta Q - Q_{20}}{C_2} = E$


$\frac{\Delta Q}{C_1} + \frac{\Delta Q}{C_2} - \frac{Q_{20}}{C_2} = E$

$\Delta Q \left(\frac{1}{C_1} + \frac{1}{C_2} \right) = E + \frac{Q_{20}}{C_2}$

$\Delta Q = \frac{E + \frac{Q_{20}}{C_2}}{\frac{1}{C_1} + \frac{1}{C_2}} = 360 \text{ mC}$

$U_1 = \frac{\Delta Q}{C_1} = 9 \text{ V}$

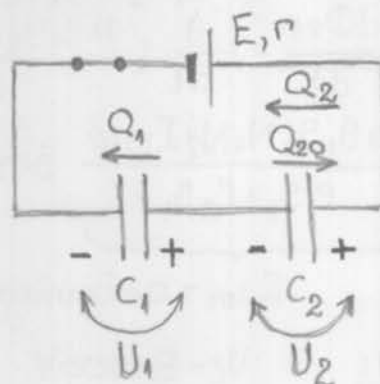$Q_2 = \Delta Q - Q_{20} = 280 \text{ mC}$




② $R_1 = R_2 = R_3 = R_4 = R_5 = R_6 = 6 \text{ m}\Omega$

$R_{DC} = ?$ $R_{23} = R_2 + R_3 = 12 \text{ m}\Omega$

$R_{234} = \frac{R_{23} \cdot R_4}{R_{23} + R_4} = 4 \text{ m}\Omega$

$R_{2346} = R_{234} + R_6 = 10 \text{ m}\Omega$

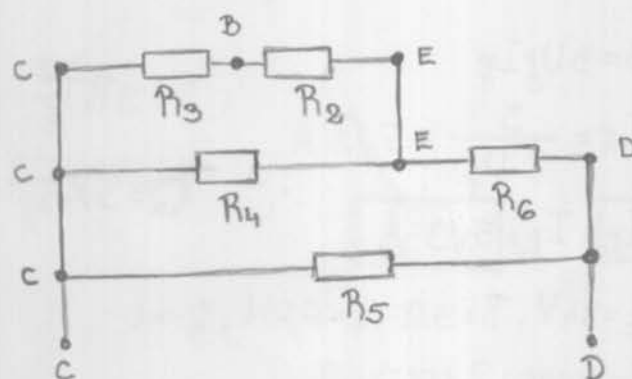$R_{DC} = \frac{R_{2346} \cdot R_5}{R_{2346} + R_5} = \frac{15}{4} \text{ m}\Omega$



③ $N_1, I_1 = 0$

$N_2, i(t) = I_m \cos(\omega t)$

$S_1, S_2, \epsilon_1, \epsilon_2, \mu$

a) $H_2 = ?$ a) 30 мФ: $\Phi = B_1 S_1 = B_2 S_2$

b) $L_2 = ?$ $B_1 = B_2 \frac{S_2}{S_1}$

b) $E_i = ?$ A3: $H_1 \epsilon_1 + H_2 \epsilon_2 = N_2 i(t)$

$H_1 = \frac{B_1}{\mu} = \frac{B_2}{\mu} \frac{S_2}{S_1}, H_2 = \frac{B_2}{\mu}$


$\frac{B_2}{\mu} \frac{S_2}{S_1} \epsilon_1 + \frac{B_2}{\mu} \epsilon_2 = N_2 i(t)$

$\frac{B_2}{\mu} \left(\frac{S_2}{S_1} \epsilon_1 + \epsilon_2 \right) = N_2 i(t)$

$\frac{B_2}{\mu} \left(\frac{\epsilon_1 S_2 + \epsilon_2 S_1}{S_1} \right) = N_2 I_m \cos(\omega t)$

$B_2 = \frac{\mu S_1 N_2 I_m \cos(\omega t)}{\epsilon_1 S_2 + \epsilon_2 S_1}$

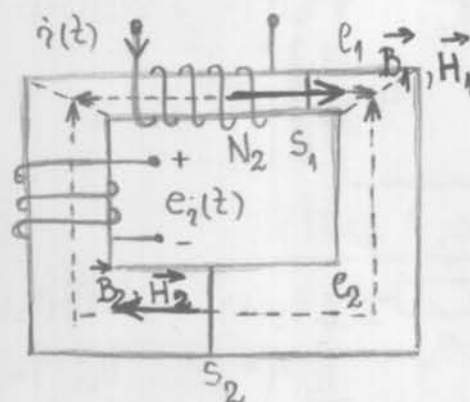$H_2 = \frac{B_2}{\mu} = \frac{S_1 N_2 I_m \cos(\omega t)}{\epsilon_1 S_2 + \epsilon_2 S_1}$



b) $\Phi_{S2} = N_2 B_1 S_1 = N_2 B_2 \frac{S_2}{S_1} S_1 = N_2 B_2 S_2$

$\Phi_{S2} = \frac{\mu S_1 S_2 N_2^2 I_m \cos(\omega t)}{\epsilon_1 S_2 + \epsilon_2 S_1}$

$L_2 = \frac{\Phi_{S2}}{i(t)} = \frac{\mu S_1 S_2 N_2^2}{\epsilon_1 S_2 + \epsilon_2 S_1}$

$$6) \Phi_{21} = N_1 B_2 S_2 = \frac{\mu S_1 S_2 N_1 N_2 I_m \cos(\omega t)}{e_1 S_2 + e_2 S_1}$$

$$e_2(t) = -\frac{d\Phi_{21}}{dt} = -\frac{d}{dt} \left(\frac{\mu S_1 S_2 N_1 N_2 I_m \cos(\omega t)}{e_1 S_2 + e_2 S_1} \right) = -\frac{\mu S_1 S_2 N_1 N_2 I_m}{e_1 S_2 + e_2 S_1} (-\sin(\omega t)) \omega$$

$$e_2(t) = \frac{\mu S_1 S_2 N_1 N_2 I_m \omega}{e_1 S_2 + e_2 S_1} \sin(\omega t), \quad [E_2] = \frac{E_{im}}{\sqrt{2}} = \frac{\mu S_1 S_2 N_1 N_2 I_m \omega}{\sqrt{2} (e_1 S_2 + e_2 S_1)}$$

E_{im} - амплитудная ЭМЭ

$$4) E = 300V$$

$$S = 4,5 \text{ kVA}$$

$$Q = 3,6 \text{ kVAR}$$

$$I_e = ?$$


$$\bar{Z} = ?$$

$$U_e = E = 300V$$

$$U_e = \sqrt{3} U_f \Rightarrow U_f = \frac{U_e}{\sqrt{3}}$$

$$U_f = 100\sqrt{3} V$$
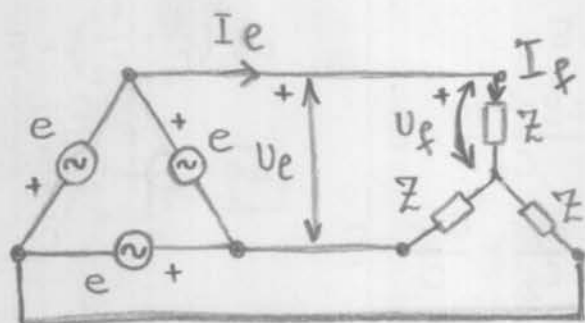
$$P = \sqrt{S^2 - Q^2} = 2,7 \text{ kW}$$



$$S = 3 U_f I_f$$

$$I_f = \frac{S}{3 U_f} = 5\sqrt{3} A$$

$$[I_e] = I_f = 5\sqrt{3} A$$


$$P = 3 R I_f^2 \Rightarrow R = \frac{P}{3 I_f^2} = 12 \Omega$$

$$Q = 3 X I_f^2 \Rightarrow X = \frac{Q}{3 I_f^2} = 16 \Omega$$

$$[\bar{Z}] = R + jX = 12 + j16 [\Omega]$$

$$5) E = 24V, R = 3\Omega, L = 6\mu H, 2 \rightarrow 1$$

a) положения 2 (CC):

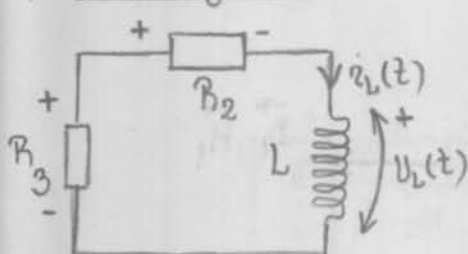

$$i_L(t) = \text{const.}$$


$$U_L(t) = 0$$

$$-R_3 i_L(t) - R_2 i_L(t) - U_L(t) = 0$$

$$-i_L(t) (R_3 + R_2) = 0 \Rightarrow i_L(t) = 0, t \leq 0$$

$$[i_L(0) = 0] \text{ по первому условию}$$

положения 1 (ПН):

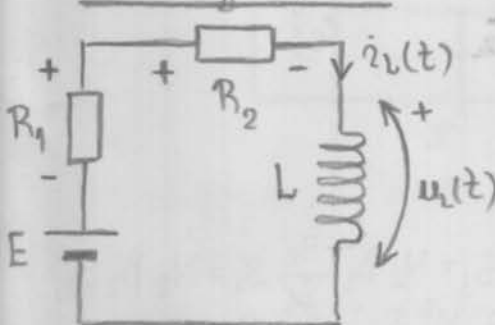

$$E - R_1 i_L(t) - R_2 i_L(t) - U_L(t) = 0 / (-1)$$

$$U_L(t) + (R_1 + R_2) i_L(t) = E, U_L(t) = L \frac{di_L(t)}{dt}$$

$$L \frac{di_L(t)}{dt} + (R_1 + R_2) i_L(t) = E / : L$$

$$\frac{di_L(t)}{dt} + \underbrace{\frac{R_1 + R_2}{L}}_{\alpha} i_L(t) = \underbrace{\left(\frac{E}{L}\right)}_{\beta}$$

$$\frac{\beta}{\alpha} = \frac{E}{R_1 + R_2} = 4A$$

$$K = ? \quad t = 0$$

$$i_L(0) = \frac{\beta}{\alpha} + K$$

$$K = i_L(0) - \frac{\beta}{\alpha} = -4A$$


$$\alpha = \frac{R_1 + R_2}{L} = 10^6 \frac{1}{s}$$

$$i_L(t) = 4 - 4e^{-10^6 t} [A], t \geq 0$$

$$U_L(t) = L \frac{di_L(t)}{dt} = 6 \cdot 10^{-6} \frac{d}{dt} (4 - 4e^{-10^6 t})$$

$$U_L(t) = 6 \cdot 10^{-6} (-4 \cdot e^{-10^6 t}) (-10^6)$$
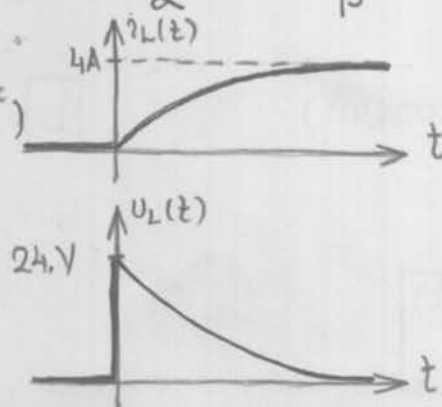
$$U_L(t) = 24 \cdot e^{-10^6 t} [V], t \geq 0$$



$$8) i_L(t_x) = 3A, t_x = ?$$

$$i_L(t_x) = 4 - 4e^{-10^6 t_x} \approx 4(1 - e^{-10^6 t_x}) = 3$$

$$1 - e^{-10^6 t_x} = \frac{3}{4}$$

$$e^{-10^6 t_x} = \frac{1}{4} / e^u$$

$$-10^6 t_x = \ln \frac{1}{4} = \ln 4^{-1} = -\ln 4$$

$$[t_x] = \frac{\ln 4}{10^6} = \ln 4 \cdot 10^{-6} s$$