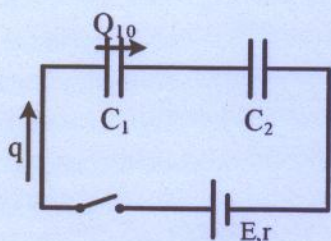



Elektrotehnika

pismeni ispit, 3.8.2025.

1. U kolu na Slici 1 prekidač je otvoren, kondenzator C_1 je opterećen početnom količinom naelektrisanja $Q_{10} = 10 \mu\text{C}$, a kondenzator C_2 je neopterećen. Poznati su parametri elemenata: $E = 5 \text{ V}$, $r = 5 \Omega$, $C_1 = 10 \mu\text{F}$ i $C_2 = 10 \mu\text{F}$. Odrediti proteklo naelektrisanje q po zatvaranju prekidača i elektrostatičke energije kondenzatora C_1 i C_2 . (10 poena)




Slika 1

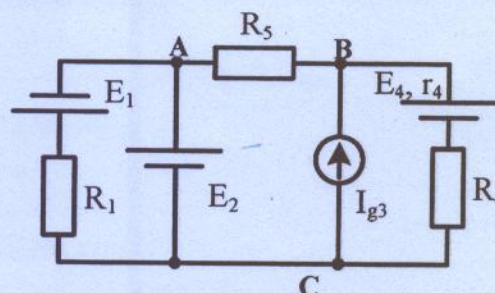

Slika 2

2. U kolu na Slici 2 poznate su vrednosti parametara elemenata: $R_1 = R_4 = R_5 = 10 \Omega$, $E_1 = 20 \text{ V}$, $E_2 = 10 \text{ V}$, $E_4 = 20 \text{ V}$, $r_4 = 5 \Omega$ i $I_{g3} = 1 \text{ A}$. Rešiti kolo primenom metode potencijala čvorova ili metode konturnih struja, a nakon toga odrediti snagu idealnog naponskog generatora E_2 . (12 poena)

3. Na Slici 3 poznata je vrednost otpornosti $R = 10 \Omega$. Kada je prekidač Π zatvoren, kroz naponski generator protiče struja $I = 3 \text{ A}$. Kada je prekidač Π otvoren, napon na krajevima realnog generatora je $U = 20 \text{ V}$. Odrediti parametre realnog naponskog generatora E i r . (8 poena)

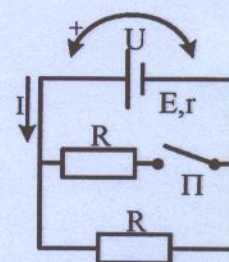


Slika 3

4. Na Slici 4 je prikazano kolo naizmenične struje koje čine naponski generator $u(t) = 100\sqrt{2} \cos(1000t) \text{ V}$ i tri potrošača poznatih vrednosti kompleksnih impedansi:

$$\bar{Z}_1 = j10 \Omega, \bar{Z}_2 = (10 + j10) \Omega \text{ i } \bar{Z}_3 = (10 - j10) \Omega.$$


- Odrediti kompleksne izraze za struje u svim granama kola. (6 p)
- Nacrtati fazorski dijagram ovih struja. (2 poena)
- Odrediti vremenski oblik struja $i_1(t)$ i $i_2(t)$. (2 poena)

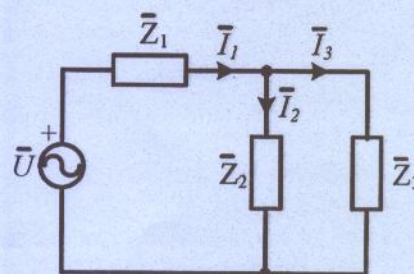

Slika 4

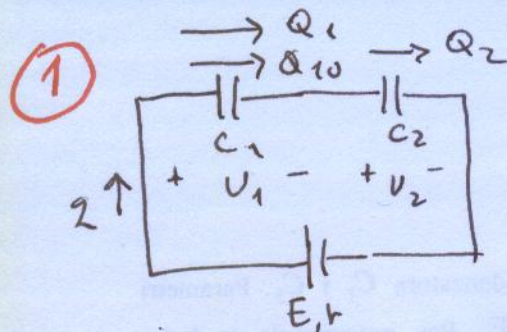5. Na naponski generator $U = 1000 \text{ V}$, $f = 50 \text{ Hz}$, priključena je paralelna veza pretežno kapacitivnog potrošača čija je aktivna snaga 50 kVA a faktor snage $4/5$ i pretežno induktivnog potrošača kroz koji protiče struja efektivne vrednosti $30\sqrt{2} \text{ A}$, a njegov faktor snage je $1/\sqrt{2}$. Odrediti:

- ukupnu aktivnu, reaktivnu i prividnu snagu paralelne veze potrošača; (6 poena)
- efektivnu vrednost struje koju paralelna veza potrošača uzima iz mreže i kompleksnu impedansu celokupnog potrošača. (4 poena)



$$Q_1 = q + Q_{10} = 30 \mu\text{C}$$

$$Q_2 = q = 20 \mu\text{C}$$

$$W_1 = \frac{1}{2} \frac{Q_1^2}{C_1} = \frac{90 \mu\text{J}}{2} = 45 \mu\text{J}$$

$$W_2 = \frac{1}{2} \frac{Q_2^2}{C_2} = \frac{400 \mu\text{J}}{2 \cdot 10 \mu} = 20 \mu\text{J}$$

$$U_1 + U_2 - E = 0$$


$$\frac{Q_1}{C_1} + \frac{Q_2}{C_2} = E$$

$$\frac{q + Q_{10}}{C_1} + \frac{q}{C_2} = E$$

$$q \left(\frac{1}{C_1} + \frac{1}{C_2} \right) = E - \frac{Q_{10}}{C_1}$$

$$q = \frac{E - Q_{10}/C_1}{1/C_1 + 1/C_2} = \frac{5 - \frac{10 \mu}{10 \mu}}{\frac{1}{10 \mu} + \frac{1}{10 \mu}}$$

$$q = 20 \mu\text{C}$$

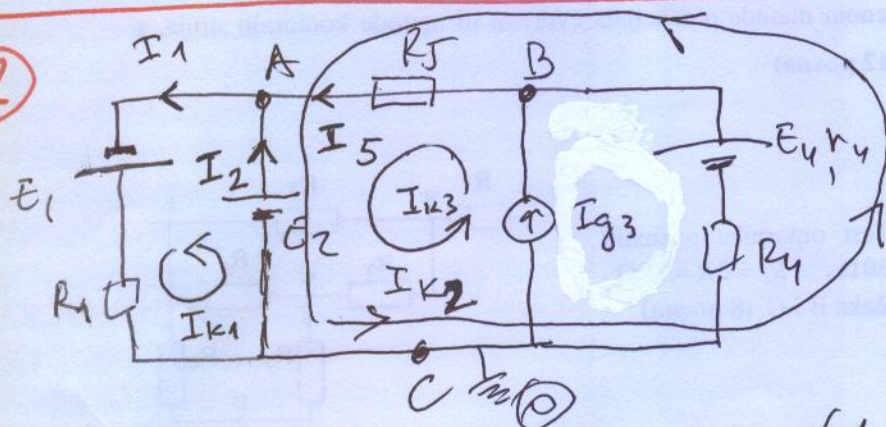

$$I_2 = I_1 - I_5$$

$$I_1 = \frac{V_A + E_1}{R_1} = \frac{10 + 20}{10} = 3 \text{ A}$$

$$I_5 = \frac{V_B - V_A}{R_5} = \frac{20 - 10}{10} = 1 \text{ A}$$

$$I_2 = 3 - 1 = 2 \text{ A}$$

$$\Rightarrow P_{E2} = E_2 I_2 = 10 \cdot 2 = 20 \text{ W}$$

MPĈ:

$$\textcircled{A} \quad V_A = E_2 = 10 \text{ V}$$

$$\textcircled{B} \quad -\frac{1}{R_5} V_A + \left(\frac{1}{R_5} + \frac{1}{R_4 + r_4} \right) V_B = I_{g3} + \frac{E_4}{R_4 + r_4}$$

$$= I_{g3} + \frac{E_4}{R_4 + r_4}$$

$$\left(\frac{1}{10} + \frac{1}{10+5} \right) V_B = 1 + \frac{20}{10+5} + \frac{10}{10}$$

$$\frac{5}{30} V_B = \frac{30+20}{15}$$

$$V_B = \frac{10}{3} \cdot 6 = 20 \text{ V}$$

MKS: $\textcircled{K1} \quad R_1 I_{K1} + 0 \cdot I_{K2} + 0 \cdot I_{K3} = E_1 + E_2$

$$\textcircled{K2} \quad 0 \cdot I_{K1} + (R_4 + r_4 + R_5) I_{K2} + R_5 I_{K3} = E_4 - E_2$$

$$\textcircled{K3} \quad I_{K3} = I_{g3} = 1 \text{ A}$$

$$I_{K1} = \frac{E_1 + E_2}{R_1} = \frac{20 + 10}{10} = 3 \text{ A}$$


$$I_{K2} = \frac{E_4 - E_2 - R_5 I_{g3}}{R_4 + r_4 + R_5} = \frac{20 - 10 - 10}{10 + 5 + 10} = \frac{0}{25} = 0 \text{ A}$$

MKS
ustavak


$$I_2 = I_{K1} - I_{K2} - I_{K3} = 3 - 0 - 1 = 2A$$

$$P_{E2} = E_2 I_2 = 20W$$

3

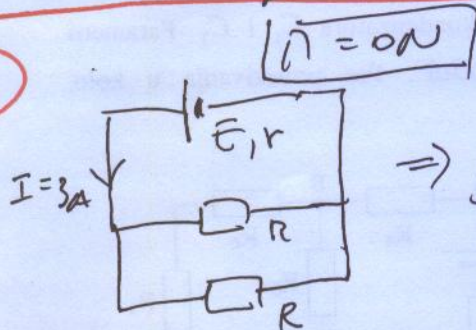

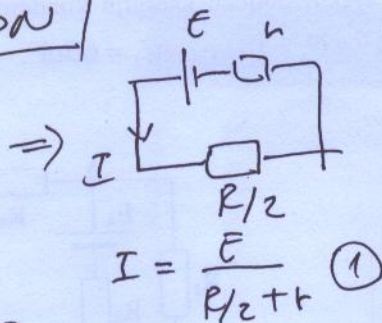
$$R \parallel R = \frac{R \cdot R}{R + R} = R/2$$



$$I = \frac{E}{R/2 + r} \quad (1)$$

h = OFF

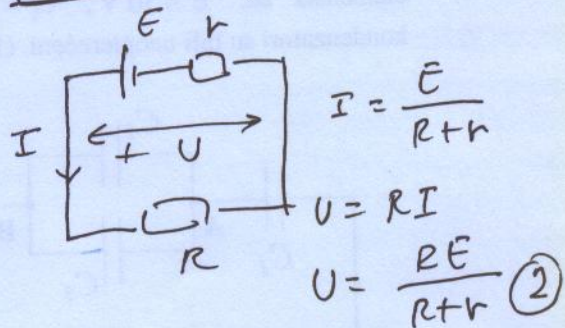

$$I = \frac{E}{R + r}$$

$$U = RI$$

$$U = \frac{RE}{R + r} \quad (2)$$

$$(1) (R/2 + r)I = E \Rightarrow (5 + r) \cdot 3 = E \Rightarrow 3r - E = -15 \quad (1)$$


$$(2) (R + r)U = RE \Rightarrow (10 + r) \cdot 20 = 10E \Rightarrow 20r - 10E = -200 \quad (2)$$

$$(2) \Rightarrow r = E/2 - 10 \quad (3)$$

$$(3), (1) \Rightarrow 3E/2 - 30 - E = -15 \Rightarrow E/2 = 15V \Rightarrow \boxed{E = 30V}$$

$$\boxed{r = 5\Omega}$$

4

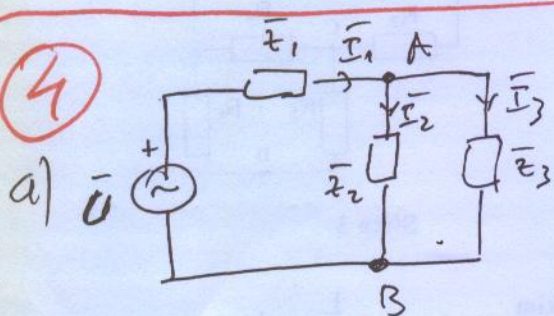

$$U = 100V$$

$$\bar{I}_2 = \frac{\bar{U}_{AB}}{\bar{Z}_2} = \frac{50\sqrt{2} e^{-j\pi/4}}{10\sqrt{2} e^{j\pi/4}}$$


$$\bar{I}_2 = 5 e^{-j\pi/2} A = -j5A$$

$$\bar{I}_3 = \frac{\bar{U}_{AB}}{\bar{Z}_3} = \frac{50\sqrt{2} e^{j\pi/4}}{10\sqrt{2} e^{-j\pi/4}}$$

$$\bar{I}_3 = 5 e^{j0} A = 5A$$

$$i_1(t) = 10 \cos(1000t - \pi/4) A$$
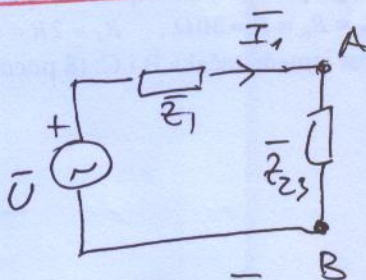
$$i_2(t) = 5\sqrt{2} \cos(1000t - \pi/2) A$$



$$\bar{U}_{AB} = \bar{Z}_{23} \cdot \bar{I}_1$$

$$\bar{I}_1 = \frac{\bar{U}}{\bar{Z}_1 + \bar{Z}_{23}}$$

$$\bar{I}_1 = \frac{100}{j10 + 10} = \frac{100}{10\sqrt{2} e^{j\pi/4}} = \frac{10}{\sqrt{2}} e^{-j\pi/4} A$$

$$\bar{U}_{AB} = \frac{100}{\sqrt{2}} e^{-j\pi/4} V = 50\sqrt{2} e^{-j\pi/4} V$$


$$\bar{Z}_{23} = \bar{Z}_2 \parallel \bar{Z}_3$$

$$\bar{Z}_{23} = \frac{\bar{Z}_2 \cdot \bar{Z}_3}{\bar{Z}_2 + \bar{Z}_3}$$


$$\bar{Z}_{23} = \frac{(10 + j10)(10 - j10)}{10 + j10 + 10 - j10}$$

$$\bar{Z}_{23} = \frac{100 + 100}{20} = 10\Omega$$

b)

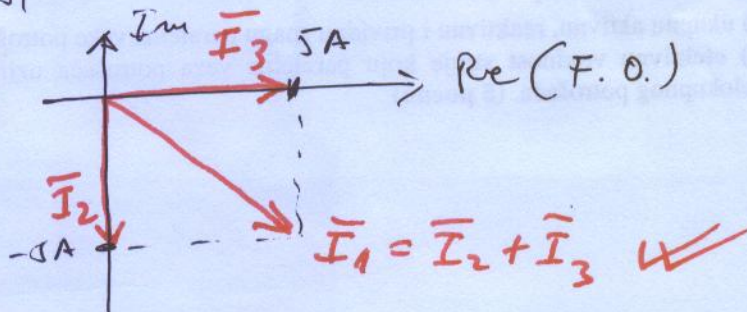

5

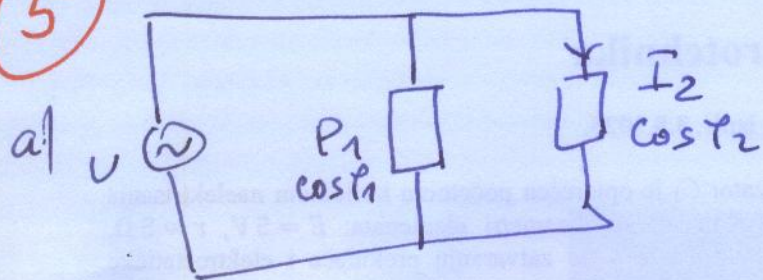

$$I_2 = 30\sqrt{2} \text{ A}$$

$$\cos \varphi_2 = \frac{1}{\sqrt{2}}$$

$\varphi_2 > 0$ INDUKTIVNI

$$\sin \varphi_2 = \sqrt{1 - \cos^2 \varphi_2}$$

$$\sin \varphi_2 = \sqrt{1 - 1/2} = \frac{1}{\sqrt{2}}$$

$$S_2 = U I_2 = 30\sqrt{2} \text{ KVA}$$

$$P_2 = S_2 \cos \varphi_2 = 30 \text{ KW}$$

$$Q_2 = S_2 \sin \varphi_2 = 30 \text{ KVAR}$$

$$P_{UK} = P_1 + P_2 = 80 \text{ KW}$$

$$Q_{UK} = Q_1 + Q_2 = 30 \text{ K} - \frac{75}{2} \text{ K} = \frac{60 \text{ K} - 75 \text{ K}}{2} = -\frac{15}{2} \text{ KVAR}$$

$$Q_{UK} = -7,5 \text{ KVAR}$$

$$S_{UK} = \sqrt{P_{UK}^2 + Q_{UK}^2} = \sqrt{80^2 + \left(-\frac{15}{2}\right)^2} = \sqrt{6400 + \frac{225}{4}}$$

$$S_{UK} = \sqrt{\frac{25600 + 225}{4}} = \frac{\sqrt{25825}}{2} \text{ KVA} (\approx 80,35 \text{ KVA})$$

UZ DIGITRON

NEOBAVEENO

NEOBAY.

UZ DIGITRON

$$b) I_{UK} = \frac{S_{UK}}{U} = \frac{\sqrt{25825}}{2000} \text{ KA} (\approx 80,35) \text{ A}$$

$$\bar{Z}_{UK} = R_{UK} + jX_{UK} \approx (12,39 + j1,16) \Omega$$

NEOBAVEENO

UZ DIGITRON

$$P_{UK} = R_{UK} I_{UK}^2 \Rightarrow R_{UK} = \frac{P_{UK}}{I_{UK}^2} = \frac{80.000}{\frac{25825}{4}} = \frac{320000}{25825} \Omega$$

$$Q_{UK} = X_{UK} I_{UK}^2 \Rightarrow X_{UK} = \frac{Q_{UK}}{I_{UK}^2} = -\frac{\frac{15000}{2}}{\frac{25825}{4}} = -\frac{30.000}{25825} \Omega$$

$$P_1 = 80 \text{ KW}$$

$$\cos \varphi_1 = 4/5$$

$\varphi_1 < 0 \Rightarrow$ KAPACITIVNI

TEKST
ZADATKA
NA ISPITU

$$\sin \varphi_1 = -\sqrt{1 - \cos^2 \varphi_1}$$

$$\sin \varphi_1 = -\sqrt{\frac{9}{25}} = -\frac{3}{5}$$

$$S_1 = \frac{50 \text{ K}}{\cos \varphi_1} = \frac{250 \text{ KVA}}{4}$$

$$S_1 = 62,5 \text{ KVA}$$

$$Q_1 = S_1 \sin \varphi_1 = -\frac{250}{4} \cdot \frac{3}{5} \text{ KVAR}$$

$$Q_1 = -\frac{150}{4} \text{ KVAR} = -37,5 \text{ KVAR}$$