


# Elektrotehnika - pismeni ispit

27. februar 2026.


1. Tačkasto naelektrisanje  $Q_1 = -Q < 0$  i veoma velika, ravnomerno naelektrisana površ, površinske gustine naelektrisanja  $\sigma_2 = \sigma > 0$  nalaze se u dielektriku relativne dielektrične permitivnosti  $\epsilon_r$  kao na Slici 1.

a) Odrediti i skicirati **vektor** elektičnog polja u tački P. (4 poena)

b) Odrediti i skicirati **vektor** sile kojom površ deluje na tačkasto naelektrisanje. (3 poena)

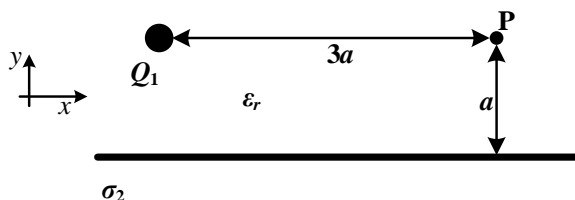


Slika 1

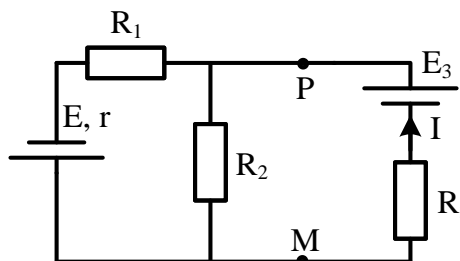


Slika 2

2. U kolu prikazanom na Slici 2, primenom Tevenenove teoreme odrediti intenzitet struje  $I$  i napon  $U_{MP}$ . Poznato je:  $E = 20\text{V}$ ,  $r = 5\Omega$ ,  $E_3 = 20\text{V}$ ,  $R_1 = 5\Omega$ ,  $R_2 = 10\Omega$ ,  $R_3 = 10\Omega$ . (10 poena)


3. U kolu sa Slike 3 potrebno je odrediti energiju kondenzatora. Poznato je:  $E = 12\text{V}$ ,  $I_g = 6\text{A}$ ,  $R_1 = R_2 = R_4 = R_5 = 4\Omega$ ,  $C_1 = 20\mu\text{F}$ . (8 poena)

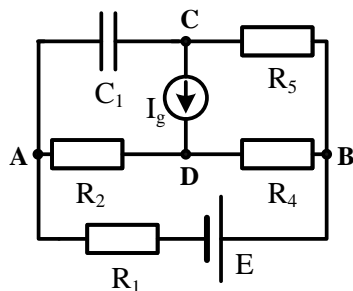

Slika 3

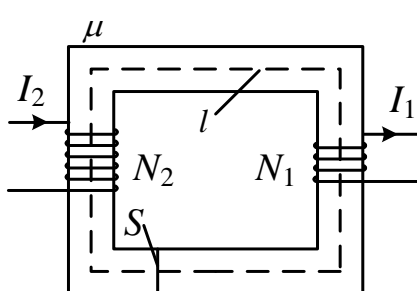

Slika 4

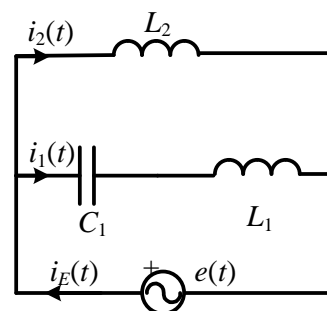

Slika 5

4. U kolu na Slici 4 prikazano je magnetno kolo sa dva namotaja. Kroz namotaj sa  $N_1 = 25$  navojaka protiče struja  $I_1 = 12\text{A}$ , a kroz namotaj sa  $N_2 = 50$  navojaka struja  $I_2 = 10\text{A}$ . Jezgro je površine poprečnog preseka  $S = 5\text{cm}^2$ , dužine srednje linije  $l = 20\text{cm}$  i magnetne permeabilnosti  $\mu = 2 \cdot 10^{-4}\text{H/m}$ .

a) Odrediti fluks vektora magnetne indukcije u jezgru. (6 poena)

b) Odrediti energiju magnetnog polja u jezgru. (4 poena)

c) Odrediti koju vrednost bi trebalo da ima struja u drugom namotaju,  $I_2' = ?$ , tako da energija magnetnog polja bude jednaka nuli. (2 poena)


5. U kolu na Slici 5 poznato je:  $e(t) = 200\sqrt{2}\cos(500t - \pi)\text{V}$ ,  $C_1 = 80\mu\text{F}$ ,  $L_1 = 40\text{mH}$ ,  $L_2 = 20\text{mH}$ . Odrediti:

a) kompleksne struje u granama i nacrtati fazorski dijagram, (5 poena)

b) vremenski oblik napona na kondenzatoru, (2 poena)

c) aktivnu, reaktivnu i prividnu snagu i faktor snage celokupnog potrošača, (4 poena)

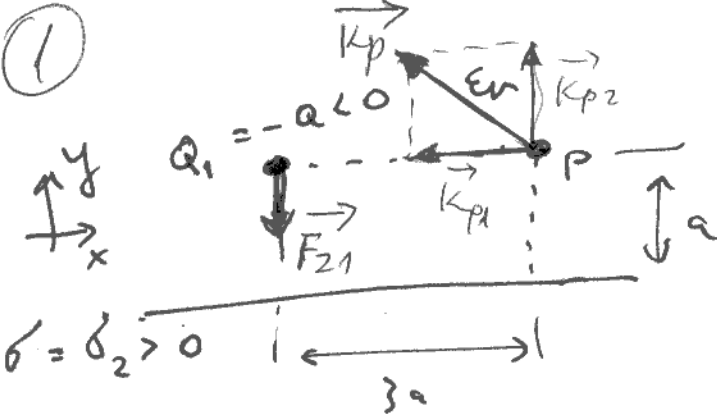d) kompleksnu admitansu potrošača. (2 poena)



a)  $\vec{K}_p = \vec{K}_{p1} + \vec{K}_{p2}$

$\vec{K}_{p1} = \frac{Q_1}{4\pi \epsilon_0 \epsilon_r (3a)^2} \vec{i}$


$\vec{K}_{p2} = \frac{-Q}{36\pi \epsilon_0 \epsilon_r a^2} \vec{i}$

$\vec{K}_{p2} = \frac{\sigma_2}{2\epsilon_0 \epsilon_r} \vec{j} = \frac{\sigma}{2\epsilon_0 \epsilon_r} \vec{j}$

$\vec{K}_p = \frac{-Q}{36\pi \epsilon_0 \epsilon_r a^2} \vec{i} + \frac{\sigma}{2\epsilon_0 \epsilon_r} \vec{j}$

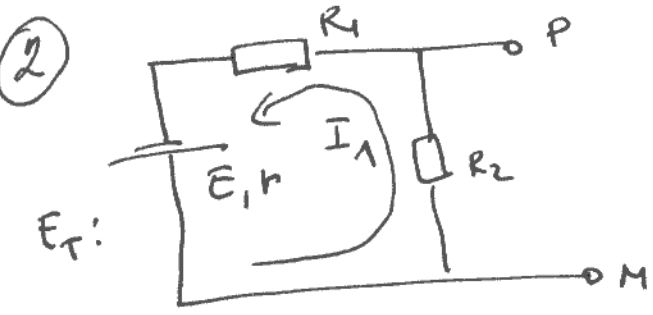b)  $\vec{F}_{21} = \vec{K}_2 \cdot Q_1 = \frac{\sigma_2 Q_1}{2\epsilon_0 \epsilon_r} \vec{j}$


$\vec{F}_{21} = -\frac{\sigma a}{2\epsilon_0 \epsilon_r} \vec{j}$



$E_T = U_{MP}$


$I_1 = \frac{E}{r + R_1 + R_2} = \frac{20}{5 + 5 + 10} = 1A$

$E_T = R_2 I_1 = 10V$

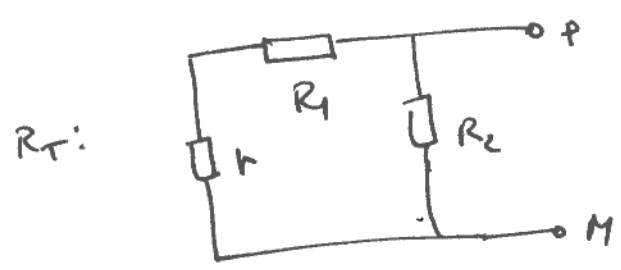


$R_T = R_{MP} = R_2 \parallel (R_1 + r) = \frac{R_2 \cdot (R_1 + r)}{r + R_1 + R_2}$

$R_T = 5 \Omega$

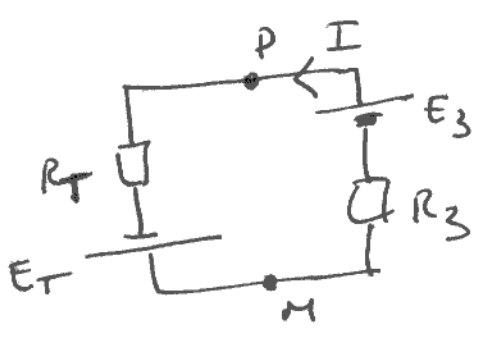

$I = \frac{E_T + E_3}{R_T + R_3} = \frac{10 + 20}{5 + 15} = 2A$

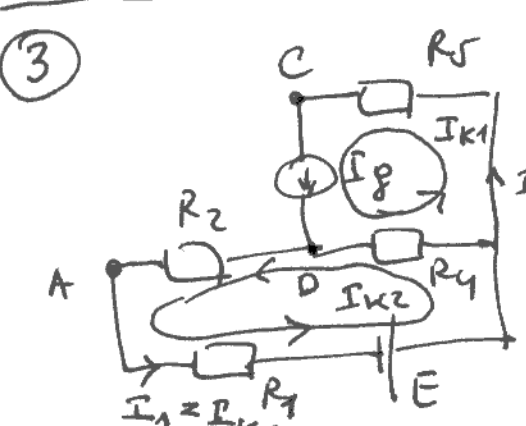$U_{MP} = -E_3 + R_3 I = -20 + 10 \cdot 2 = 0V$



(1)  $I_{K1} = I_g = 6A$

(2)  $R_{21} I_{K1} + R_{22} I_{K2} = \sum_{k2} E_i$

$-R_4 I_g + (R_1 + R_2 + R_4) I_{K1} = E$


$I_{K2} = \frac{E + R_4 I_g}{R_1 + R_2 + R_4} = \frac{12 + 4 \cdot 6}{4 + 4 + 4} = 3A$

$U_{CA} = U_{AC} = R_1 I_1 - E + R_5 I_5 = 24V$

$$W_{C1} = \frac{1}{2} C_1 \cdot U_{C1}^2 = \frac{1}{2} \cdot 20 \cdot 10^{-6} \cdot \underbrace{(24)^2}_{576} = 5760 \mu\text{J} = 5,76 \text{ mJ}$$

4

a)

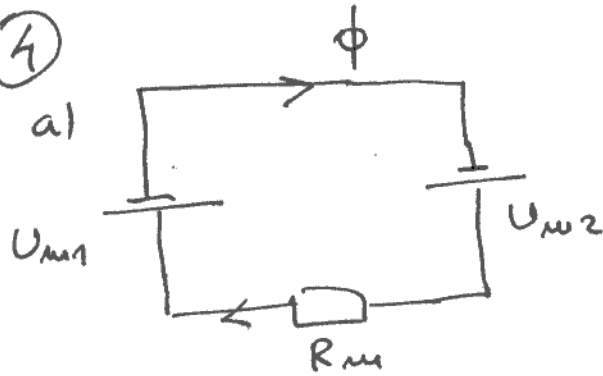

$$U_{m1} = N_1 I_1$$

$$U_{m2} = N_2 I_2$$

$$R_{m1} = \frac{l}{\mu S}$$

$$S = 5 \text{ cm}^2 = 5 \cdot (10^{-2})^2 \text{ m}^2$$

$$S = 5 \cdot 10^{-4} \text{ m}^2$$

$$l = 20 \text{ cm} = 0,2 \text{ m}$$

$$\phi = \frac{U_{m2} - U_{m1}}{R_{m1}} = \frac{N_2 I_2 - N_1 I_1}{\frac{l}{\mu S}}$$

b)  $B = \frac{\phi}{S} = \frac{100 \mu\text{Wb}}{5 \cdot 10^{-4}} = 0,2 \text{ T}$

$$\phi = \frac{50 \cdot 10 - 25 \cdot 12}{\frac{0,2}{2 \cdot 10^{-4} \cdot 5 \cdot 10^{-4}}} = \frac{200}{2 \cdot 10^6} = 100 \mu\text{Wb}$$

$$B = 0,2 \text{ T}$$

$$H = \frac{B}{\mu} = \frac{0,2}{2 \cdot 10^{-4}} = 1000 \frac{\text{A}}{\text{m}}$$

$$W_m = \frac{1}{2} B H \Rightarrow W_m = \frac{B H \cdot S l}{2} = \frac{0,2 \cdot 10^3 \cdot 5 \cdot 10^{-4} \cdot 0,2}{2}$$

$$W_m = 10 \text{ mJ}$$

c)  $W'_m = 0 \Rightarrow B' = 0, H' = 0 \Rightarrow \phi' = 0 \Rightarrow N_1 I_1 = N_2 I_2'$   

$$I_2' = \frac{N_1}{N_2} I_1 = 6 \text{ A}$$

5 a)  $\bar{E} = 200 e^{j\omega t} \cdot r = -200 \text{ V}$

$$\bar{Z}_{L1} = j\omega L_1 = j500 \cdot 40 \text{ m} = j20 \Omega$$


$$\bar{Z}_{L2} = j\omega L_2 = j500 \cdot 20 \text{ m} = j10 \Omega$$

$$\bar{Z}_{C1} = -j \frac{1}{\omega C_1} = -j \frac{1}{500 \cdot 80 \mu} = -j \frac{10^6}{40 \cdot 10^3} = -j25 \Omega$$

$$\bar{I}_1 = \frac{\bar{E}}{\bar{Z}_{L1} + \bar{Z}_{C1}} = \frac{-200}{j20 - j25} = \frac{-200}{-j5} = -j40 \text{ A} = 40 e^{j\pi/2} \text{ A}$$

$$\bar{I}_2 = \frac{\bar{E}}{\bar{Z}_{L2}} = \frac{-200}{j10} = j20 \text{ A} = 20 e^{j\pi/2} \text{ A}$$
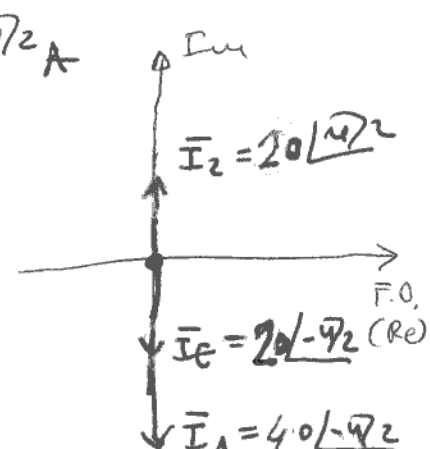
$$\bar{I}_E = \bar{I}_1 + \bar{I}_2 = -j40 + j20 = -j20 \text{ A}$$



$$b) \bar{U}_{e1} = \bar{Z}_{e1} \cdot \bar{I}_1 = (-j25) \cdot (-j40) = -1000 \text{ V} = 1000 e^{-j\pi} \text{ V}$$

$$u_{e1}(t) = 1000\sqrt{2} \cos(500t - \pi) \text{ V}$$

$$c) \bar{S}_p = \bar{S}_q = \bar{E} \bar{I}_E^* = -200 \cdot (-j20)^* = -200 \cdot (j20)$$

$$\bar{S}_p = (-j4000) \text{ VA}$$

$$P = 0 \text{ W}, \quad Q = -4 \text{ kVAR}, \quad S = 4 \text{ kVA}$$

$$\cos \varphi = \frac{P}{S} = 0$$

$$d) \bar{Y}_e = \bar{Y}_1 + \bar{Y}_2$$

$$\bar{Y}_1 = \frac{1}{\bar{Z}_1} = \frac{1}{\bar{Z}_1 + \bar{Z}_{e1}} = \frac{1}{-j5} = j0,2 \text{ S}$$

$$\bar{Y}_2 = \frac{1}{\bar{Z}_2} = \frac{1}{\bar{Z}_2} = \frac{1}{j10} = -j0,1 \text{ S}$$

$$\bar{Y}_e = j0,2 - j0,1 = j0,1 \text{ S}$$